

6. Complex Power in AC Circuits

Introduction to Electric Circuits Supplemental Instruction

Cooper McAllister

April 16 2026

This document is not a substitute for a textbook or classroom instruction. It may contain errors and is intended to be used only to the extent that it is helpful to supplement students' learning experience.

1 Introduction

2 RMS Values

When we analyze the power of AC circuits, we use **RMS values**, which give the effective value of a sinusoidal voltage or current. For a sinusoidal voltage $\mathbf{V} = V_m \angle \alpha_v$ or current $\mathbf{I} = I_m \angle \alpha_i$, the RMS value is

$$V_{rms} = \frac{V_m}{\sqrt{2}} \quad I_{rms} = \frac{I_m}{\sqrt{2}}$$

3 Average (True) Power

For a component or network, given $\mathbf{V} = V_m \angle \alpha_v$ and $\mathbf{I} = I_m \angle \alpha_i$, the **average power** is:

$$P = V_{rms} I_{rms} \cos(\alpha_v - \alpha_i)$$

Or, using magnitudes,

$$P = \frac{V_m I_m}{2} \cos(\alpha_v - \alpha_i)$$

Average power is sometimes also called **true power** or **real power**. The **unit** of average power is Watts (W). Average power is associated with resistance.

4 Reactive Power

For a component or network, given $\mathbf{V} = V_m \angle \alpha_v$ and $\mathbf{I} = I_m \angle \alpha_i$, the **reactive power** is:

$$Q = V_{rms} I_{rms} \sin(\alpha_v - \alpha_i)$$

Or, using magnitudes,

$$Q = \frac{V_m I_m}{2} \sin(\alpha_v - \alpha_i)$$

The **unit** of average power is Volt Amps Reactive (VAR). Reactive power is associated with reactive components (inductors and capacitors).

5 Apparent Power

For a component or network, given $\mathbf{V} = V_m \angle \alpha_v$ and $\mathbf{I} = I_m \angle \alpha_i$, the **apparent power** is:

$$S = V_{rms} I_{rms}$$

Or, using magnitudes,

$$S = \frac{V_m I_m}{2}$$

The **unit** of apparent power is Volt Amps (VA).

6 Power Factor

For a component or network, given $\mathbf{V} = V_m \angle \alpha_v$ and $\mathbf{I} = I_m \angle \alpha_i$, the **power factor** is:

$$PF = \cos(\alpha_v - \alpha_i)$$

Power factor is specified as either leading or lagging, describing whether the current leads or lags the voltage. If $\alpha_i > \alpha_v$, the power factor is leading; if $\alpha_i < \alpha_v$, the power factor is lagging.

7 Complex Power and the Power Triangle

In summary, we have

$$P = V_{rms} I_{rms} \cos(\alpha_v - \alpha_i)$$

$$Q = V_{rms} I_{rms} \sin(\alpha_v - \alpha_i)$$


$$S = V_{rms} I_{rms}$$

$$PF = \cos(\alpha_v - \alpha_i)$$

Complex power is

$$\mathbf{S} = P + jQ = S \angle (\alpha_v - \alpha_i)$$

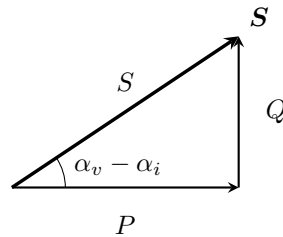We can draw this as a triangle in the complex plane, where average power is the horizontal component, reactive power is the vertical component, and apparent power is the magnitude:



References

- M. Iordache. Class Lectures, Topic: “Electric circuits.” EEGR 2053, School of Engineering and Engineering Technology, LeTourneau University, 2025.
- M. Iordache. 2024. EEGR 2053 Electric circuits [PowerPoint slides]. Available: <https://mviordache.name/EEGR2053/index.html>
- T. L. Floyd and D. M. Buchla, Principles of Electric Circuits: Conventional Current, 10th ed. Hoboken, NJ: Pearson Education, 2020.
- O. Ortiz. 2025. ENGR 2053 Intro to electric circuits [PowerPoint slides].