

Operational Amplifiers


Introduction to Electric Circuits

Supplemental Instruction


Cooper McAllister

September 21 2026

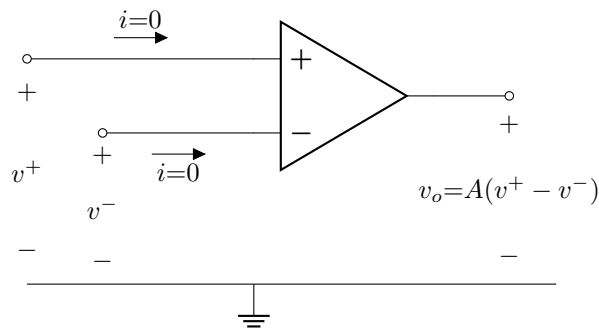An Operational Amplifier is commonly drawn with the following symbol:



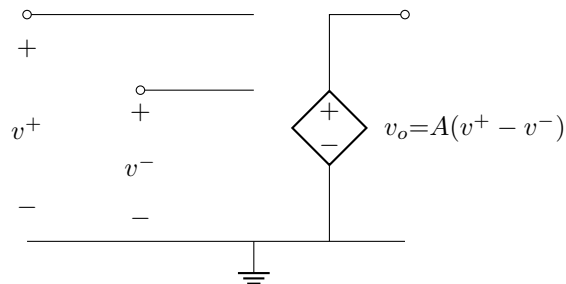It can be replaced with the following circuit:



An important note is that for the first symbol, the supply power connections to the op amp are not shown, so **KCL cannot be applied** to a network that includes the op amp:

